
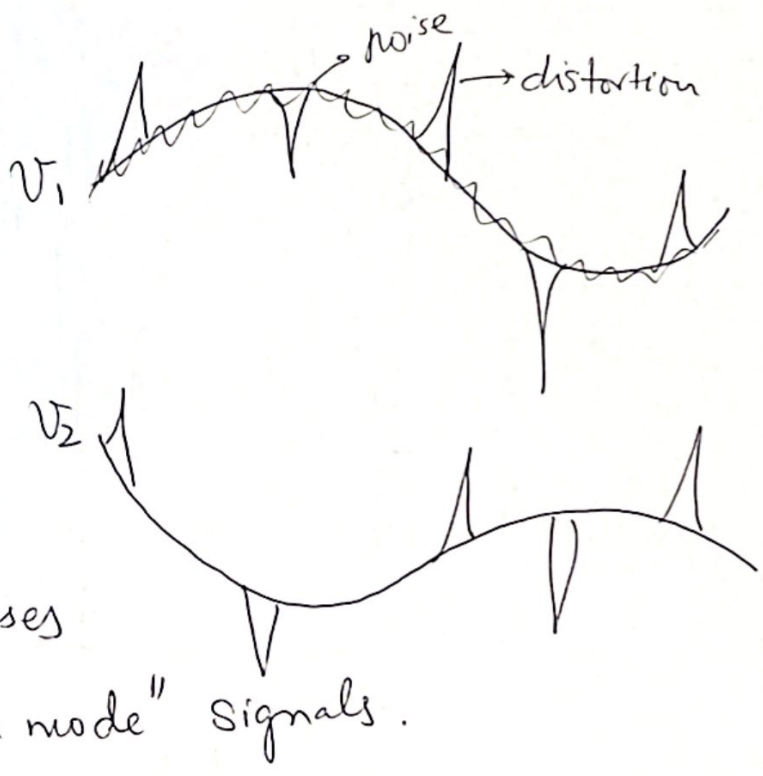


Lec 25 Differential Amplifiers


Common mode noise & distortion

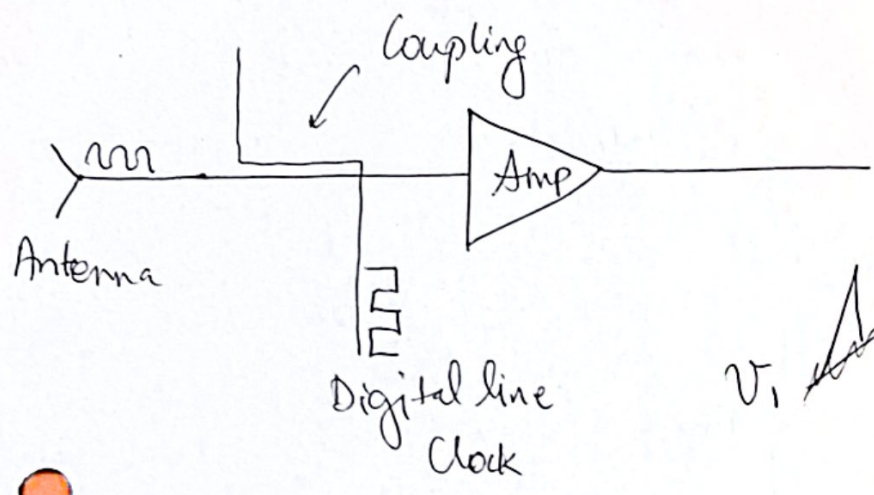

> Fix? Differential Signals.

$V_d = V_1 - V_2 \Rightarrow$ Suppresses "Common mode" signals.

Implementation?

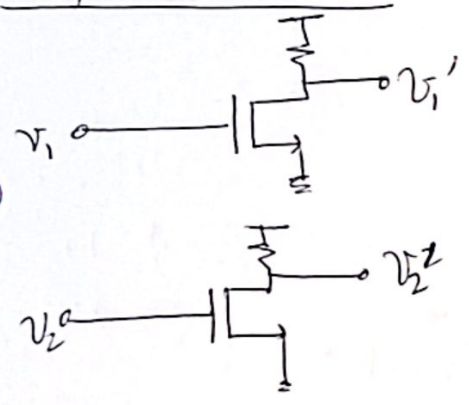

Is this good enough?

No because this also amplifies the common mode.

> Differential & common mode representation.


Given $V_1, V_2 \Rightarrow V_c = \frac{V_1 + V_2}{2} \rightarrow$ Common mode

$V_1 = \frac{V_d}{2} + V_c$ $V_d = V_1 - V_2 \rightarrow$ Differential mode.

$V_2 = V_c - \frac{V_d}{2}$

We want V_d to have gain & V_c to have loss!

Solution: Differential amplifier.

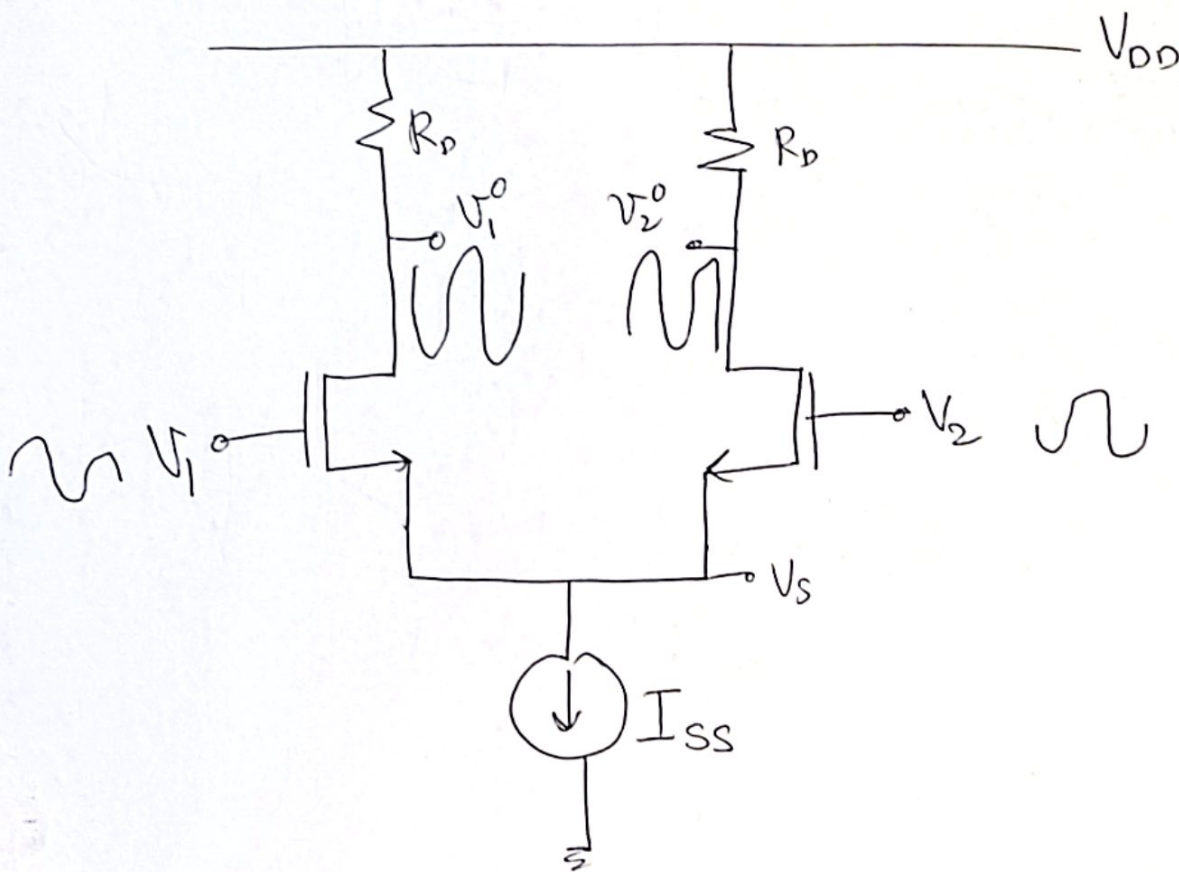

$V_1 \uparrow$ & $V_2 \downarrow \Rightarrow I_{SS}$ is steered in branch ①

$V_2 \uparrow$ & $V_2 \uparrow \Rightarrow$ Current cannot change $\rightarrow V_S \uparrow$ to keep V_{GS} constant. (In reality I_{SS} is not ideal)

Large Signal Analysis

$$\left. \begin{aligned} V_{GS1} &= V_1 - V_S \\ V_{GS2} &= V_2 - V_S \end{aligned} \right\} \Rightarrow V_{GS1} - V_{GS2} = V_1 - V_2 = V_d$$

$$I_{D1} = \frac{1}{2} \underbrace{\mu_n C_{ox} \frac{W}{L}}_{k'} (V_{GS1} - V_T)^2$$


$$\Rightarrow V_{GS1} = V_T + \sqrt{\frac{I_{D1}}{k'}}$$

$$\Delta I = I_{D1} - I_{D2}$$

$$I_{SS} = I_{D1} + I_{D2}$$

$$\Rightarrow I_{D1} = \frac{I_{SS} + \Delta I}{2}$$

$$I_{D2} = \frac{I_{SS} - \Delta I}{2}$$

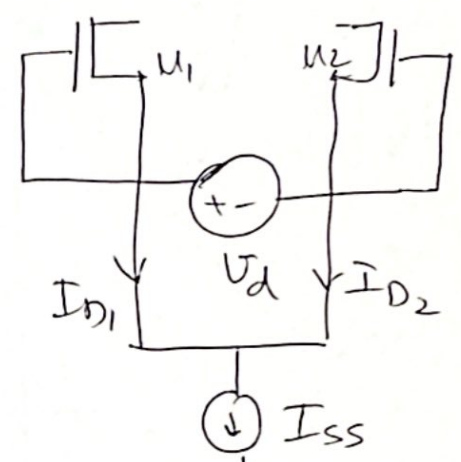

$$V_d = V_T + \sqrt{\frac{I_{D1}}{k'}} - V_T - \sqrt{\frac{I_{D2}}{k'}}$$

[If $M_1 = M_2 \Rightarrow V_T$ cancels & k' is the same]


$$V_d = \frac{1}{\sqrt{2k'}} \left[\sqrt{I_{SS} + \Delta I} - \sqrt{I_{SS} - \Delta I} \right]$$

$$\begin{aligned} \Rightarrow 2k' V_d^2 &= I_{SS} + \Delta I + I_{SS} - \Delta I - 2 \sqrt{I_{SS}^2 - \Delta I^2} \\ &= 2 I_{SS} - 2 \sqrt{I_{SS}^2 - \Delta I^2} \end{aligned}$$

$$\Rightarrow \sqrt{I_{SS}^2 - \Delta I^2} = I_{SS} - k' \Delta V_i^2 \quad \Delta V_i = V_d$$

$$\Rightarrow I_{SS}^2 - \Delta I^2 = I_{SS}^2 + k'^2 \Delta V_i^4 - 2k' \Delta V_i^2 I_{SS}$$
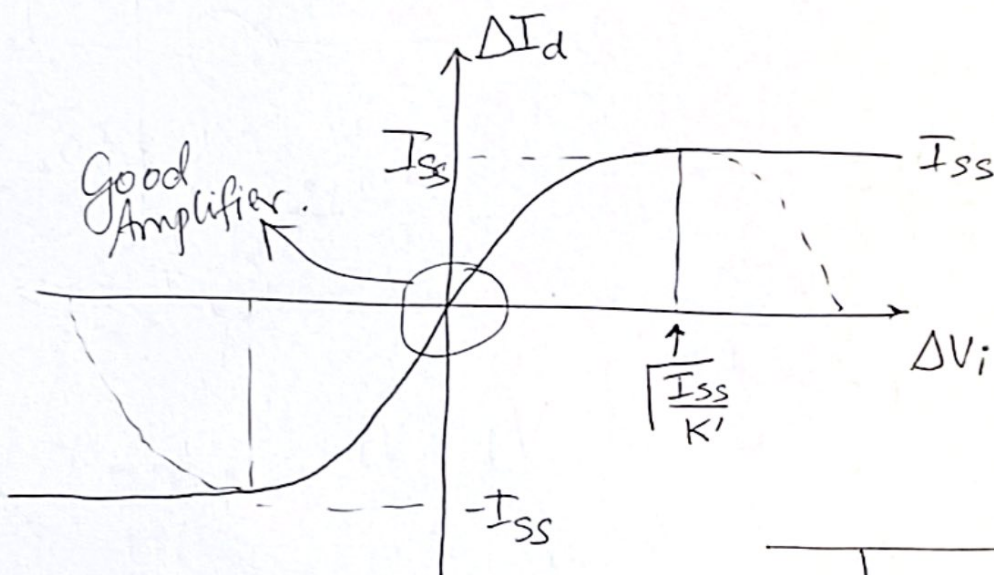
$$\Rightarrow \Delta I_d = k' \Delta V_i \sqrt{\frac{2I_{SS}}{k'} - \Delta V_i^2}$$




$$I_{SS} = k' \cancel{V_{GS}^2} (V_{GS} - V_T)^2$$



$$\Rightarrow V_{GS1} = V_T + \sqrt{\frac{I_{SS}}{k'}}$$

$$\Rightarrow \Delta V_i = \sqrt{\frac{I_{SS}}{k'}}$$

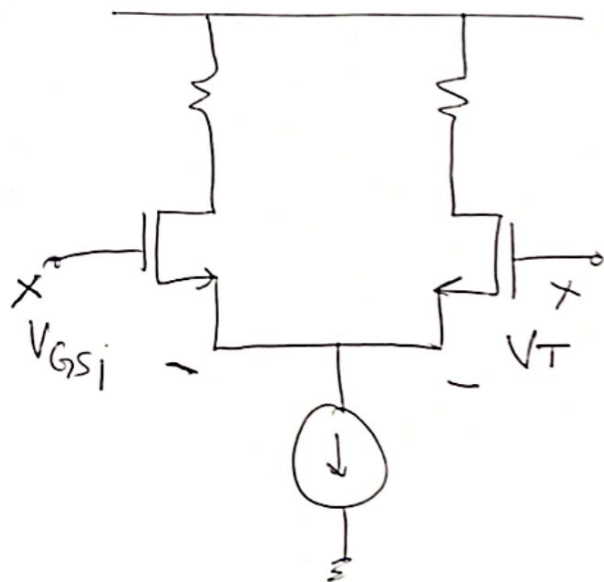→ In reality there is subthreshold current.



Small Signal Analysis

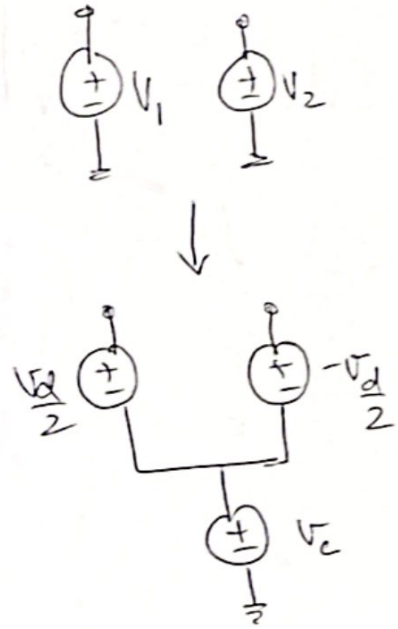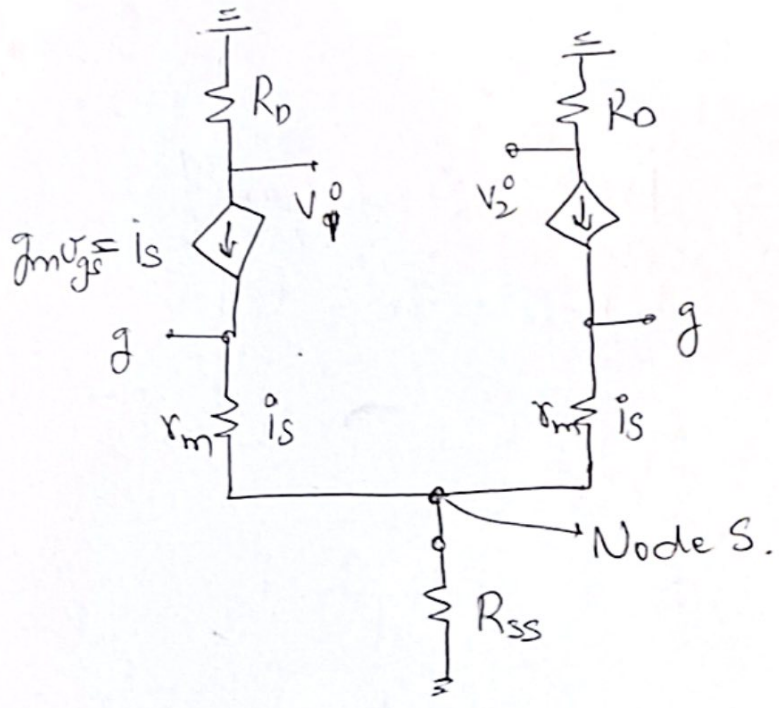


Differential mode / odd mode

> V_d is applied.


⇒ Node S is always at 0 voltage. (Note this is "small signal" analysis so we ignore bias points.)

⇒ Each half circuit is

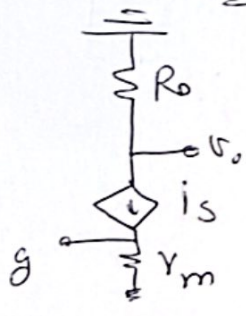

~~Source degeneration.~~



⇒ Common Source! ⇒ $A_v = -g_m R_D$

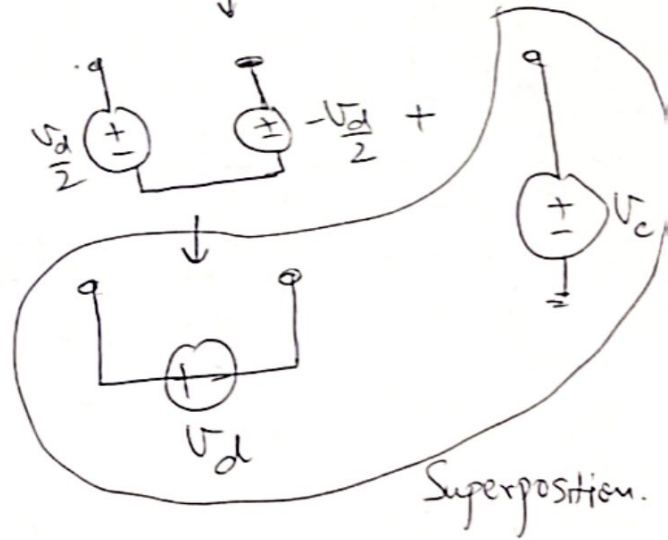

$$\frac{V_{od}/2}{V_{id}/2} = A_v = -g_m R_D$$

$\Rightarrow A_{vd} \left[\frac{V_{od}}{V_{id}} = -g_m R_D \right] \rightarrow$ Differential gain!
 But note g_m is half

Common Mode

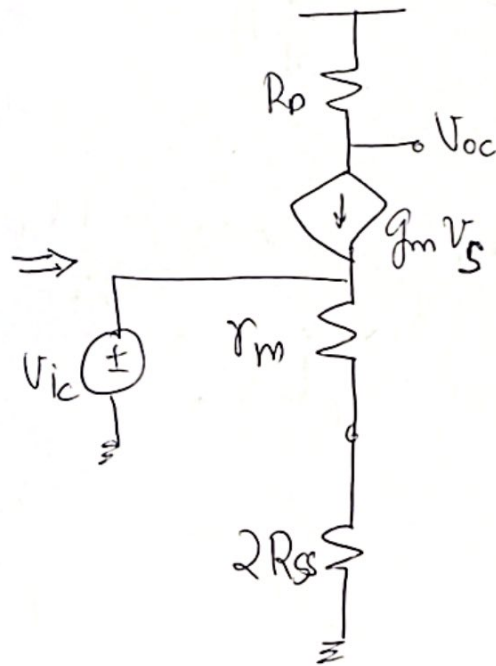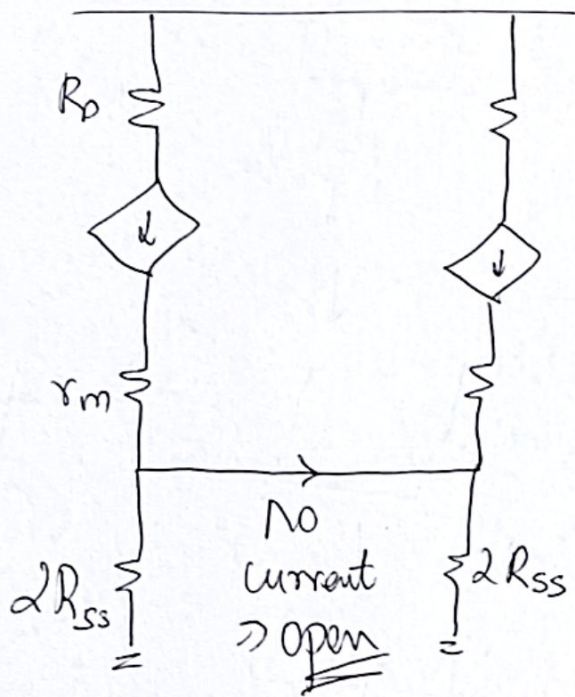

$$\Rightarrow A_{vc} \left[\frac{V_{oc}}{V_{ic}} = \frac{-g_m R_D}{1 + 2g_m R_{SS}} \right]$$

$$CMRR = \frac{-g_m R_D}{-g_m R_D / (1 + 2g_m R_{SS})} = 1 + 2g_m R_{SS}$$

Note $R_{SS} \uparrow \Rightarrow$
 $\Rightarrow CMRR \infty$